

Creating a traffic light controller in Tinkercad is a great way to learn how to simulate a simple Arduino project. Here's a step-by-step guide to creating a traffic light system using three LEDs (red, yellow, and green):

Step 1: Create a New Tinkercad Project

1. Log in to Tinkercad or create an account if you haven't already.
2. Click on "Create New Circuit" to start a new project.

Step 2: Add Components

1. In the Components panel on the right, search for and add the following components to your workspace:
 - Arduino Uno
 - 3 LEDs (Red, Yellow, and Green)
 - 3 220-ohm resistors (one for each LED)
 - 3 push-button switches
2. Arrange the components on your workspace and wire them as follows:
 - Connect the longer leg (anode) of each LED to a 220-ohm resistor. Connect the other end of each resistor to a different digital pin on the Arduino (e.g., 2, 3, and 4).
 - Connect the shorter leg (cathode) of each LED to a common ground rail on your breadboard.
 - Connect one terminal of each push-button switch to a different digital pin on the Arduino (e.g., 5, 6, and 7).
 - Connect the other terminal of each push-button switch to a common ground rail on your breadboard.

Your setup should look something like this:

Step 3: Write the Arduino Code

1. Click on the Arduino Uno board to open the code editor.
2. Copy and paste the following Arduino code:

```
arduinoCopy code
// Define the pin numbers for the LEDs
int redLED = 2;
int yellowLED = 3;
int greenLED = 4;

// Define the pin numbers for the push-button switches
int redButton = 5;
int yellowButton = 6;
int greenButton = 7;
```

```

void setup() {
  // Set LED pins as OUTPUT
  pinMode(redLED, OUTPUT);
  pinMode(yellowLED, OUTPUT);
  pinMode(greenLED, OUTPUT);

  // Set button pins as INPUT_PULLUP
  pinMode(redButton, INPUT_PULLUP);
  pinMode(yellowButton, INPUT_PULLUP);
  pinMode(greenButton, INPUT_PULLUP);
}

void loop() {
  // Check the state of each button
  int redState = digitalRead(redButton);
  int yellowState = digitalRead(yellowButton);
  int greenState = digitalRead(greenButton);

  // Traffic light control logic
  if (redState == LOW) {
    // Red light
    digitalWrite(redLED, HIGH);
    digitalWrite(yellowLED, LOW);
    digitalWrite(greenLED, LOW);
  } else if (yellowState == LOW) {
    // Yellow light
    digitalWrite(redLED, LOW);
    digitalWrite(yellowLED, HIGH);
    digitalWrite(greenLED, LOW);
  } else if (greenState == LOW) {
    // Green light
    digitalWrite(redLED, LOW);
    digitalWrite(yellowLED, LOW);
    digitalWrite(greenLED, HIGH);
  } else {
    // All lights off
    digitalWrite(redLED, LOW);
    digitalWrite(yellowLED, LOW);
    digitalWrite(greenLED, LOW);
  }
}

```

Step 4: Simulate and Test

1. Click the "Start Simulation" button to run your simulation.
2. Press the push-button switches to change the traffic light sequence. Each button corresponds to a different traffic light state.
3. Observe how the LEDs change their states based on the button presses. You should see the traffic light sequence (Red -> Yellow -> Green) in response to the button presses.

That's it! You've successfully created a traffic light controller in Tinkercad. This project helps you understand the basics of input and output control using Arduino and simulates a simple traffic light system. You can further expand on this project by adding features like pedestrian crossing signals or a timer.

